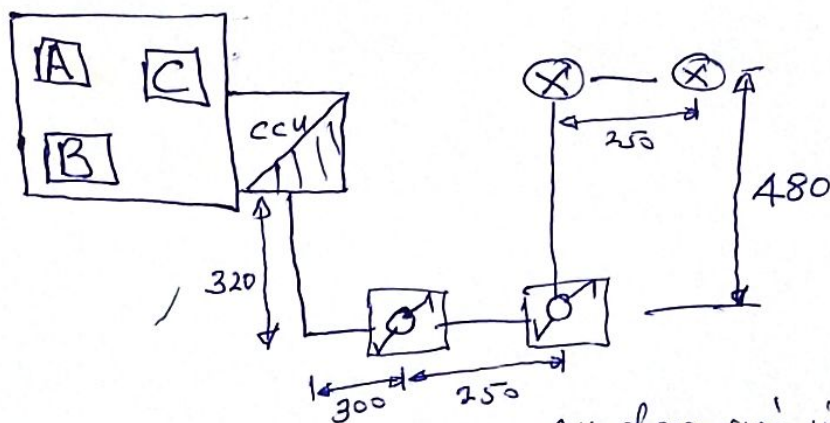


Exercise 2: Final Circuit

CBET/DCBET 245/6.

The fig below shows a layout of two lamps controlled from two independent positions and a Consumer intake position.



All dimensions in millimetres.

Procedure:

(a) Draw a wiring diagram for the installation such that:

- i) the intake position is wired in the correct sequence;
- ii) The two lamps L_1 and L_2 are controlled from two independent positions ~~so~~ to operate simultaneously.

(b) List down all the materials and components required for the installation.

(c) List down the relevant tools for the installation.

(d) Complete the wiring of the installation in pvc sheathed cables.

(e) Power the completed installation to test operation.

— x — x — P.m. Ithin