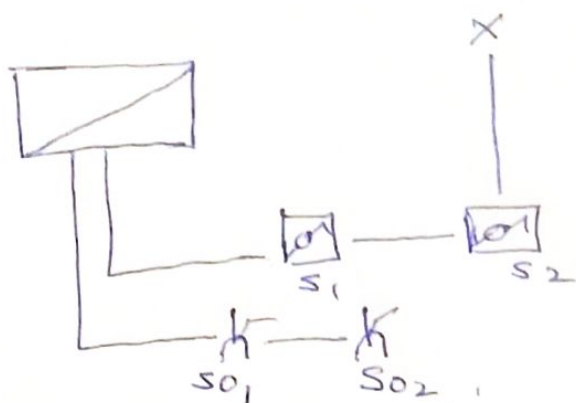


Assignment - Machine & System Maintenance

Regarding the below outlined layout diagram, draw the wiring diagram for the installation and answer the questions below attached.



Procedure 1) The lamp is controlled from the two independent positions.

- 2) Socket outlets are wired in radial.
- 3) Wiring to be done in pvc sheathed cables.

Maintenance Questions

- ① Outline possible causes that would cause the lamp fail to operate.
- 2) The lamp operates by switch S1 only such that S2 is a slave of S1. Outline possible causes of this situation.
- 3) State possible causes of socket outlet SO2 losing power when SO2 is fully powered.
- ④ Draw wiring diagram as describe in procedure ① and ②.

— X — X —